

G9 Science: Class 13 Homework

1. The total resistance of the circuit below is $25\ \Omega$. The voltage across the battery is 6.0V .


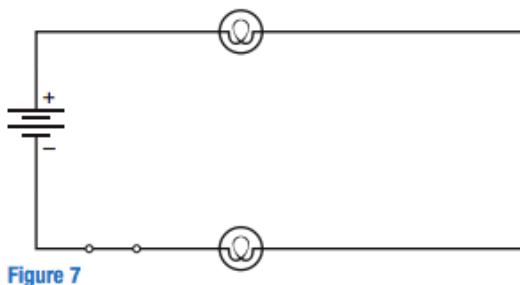



Figure 7

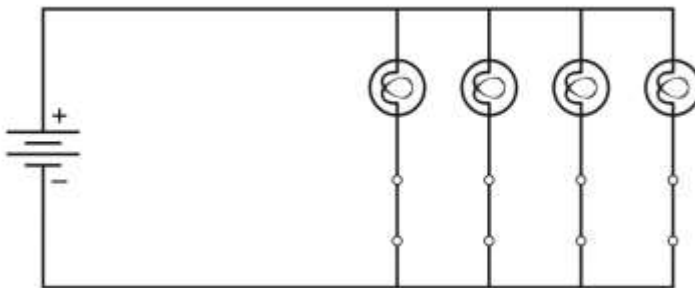- a. Calculate the current in the circuit. **[3 marks]**
- b. Calculate the voltage drop across each lamp. **[2 marks]**
2. A house has a lamp in every room. The circuit for the lamps is shown below. The voltage drop across the energy source is 120V . The total resistance is 10Ω .




- a. Calculate the current through each lamp. **[3 marks]**
- b. Calculate the voltage drop across each lamp. **[1 mark]**

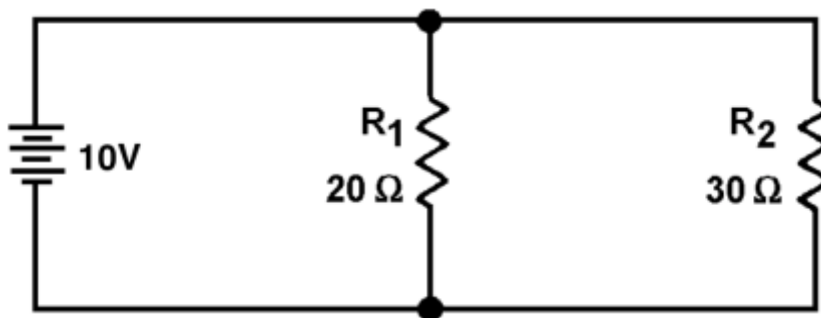
3. What would happen to the voltage drop across each lamp if you kept adding lamps to a series circuit? Explain your answer. **[3 marks]**
4. A battery-powered set of five patio lanterns is connected in series. An ammeter measures the current through the battery as 0.75A. The total resistance of the circuit is 52Ω .
- a. Calculate the voltage drop across the battery. **[3 marks]**
- b. Calculate the voltage drop across each load. **[3 marks]**
5. Find the potential difference and current for each resistor in the following circuit. **[4 marks]**



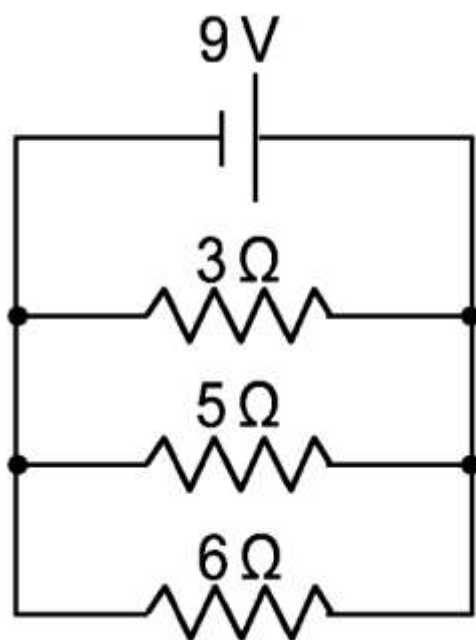6. Find the potential difference and current for each resistor in the following diagram.
[6 marks]



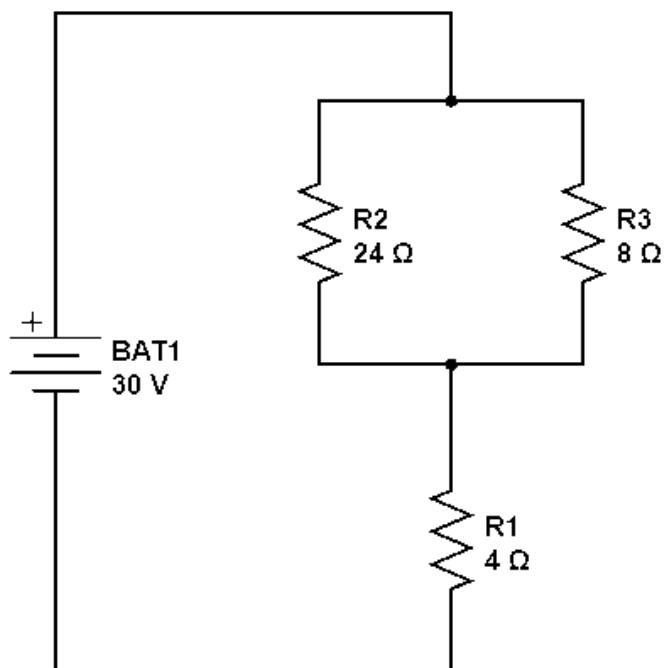7. Find the potential difference and current for each resistor in the following diagram.
[6 marks]



8. Find the potential difference and current for each resistor in the following diagram.
[10 marks]

